



Palestine Technical University-Kadoorie

High Level Digital Design

1214-0420

Term Project

Three 4-bit numbers adder

Prepared by:

Mohammad Saleh AbuSafat

Supervisor:

Dr. Mahmoud Moshref


Project submitted in VHDL Course Requirement for the Bachelor Degree

2021/2022

**Objective:** Design a three 4-bit numbers adder.

**Details of the design:** Ripple Carry Adder (RCA) performs addition of two  $n$ -bit numbers. Therefore, the adder shown in the figure below performs the addition in two stages as follows:

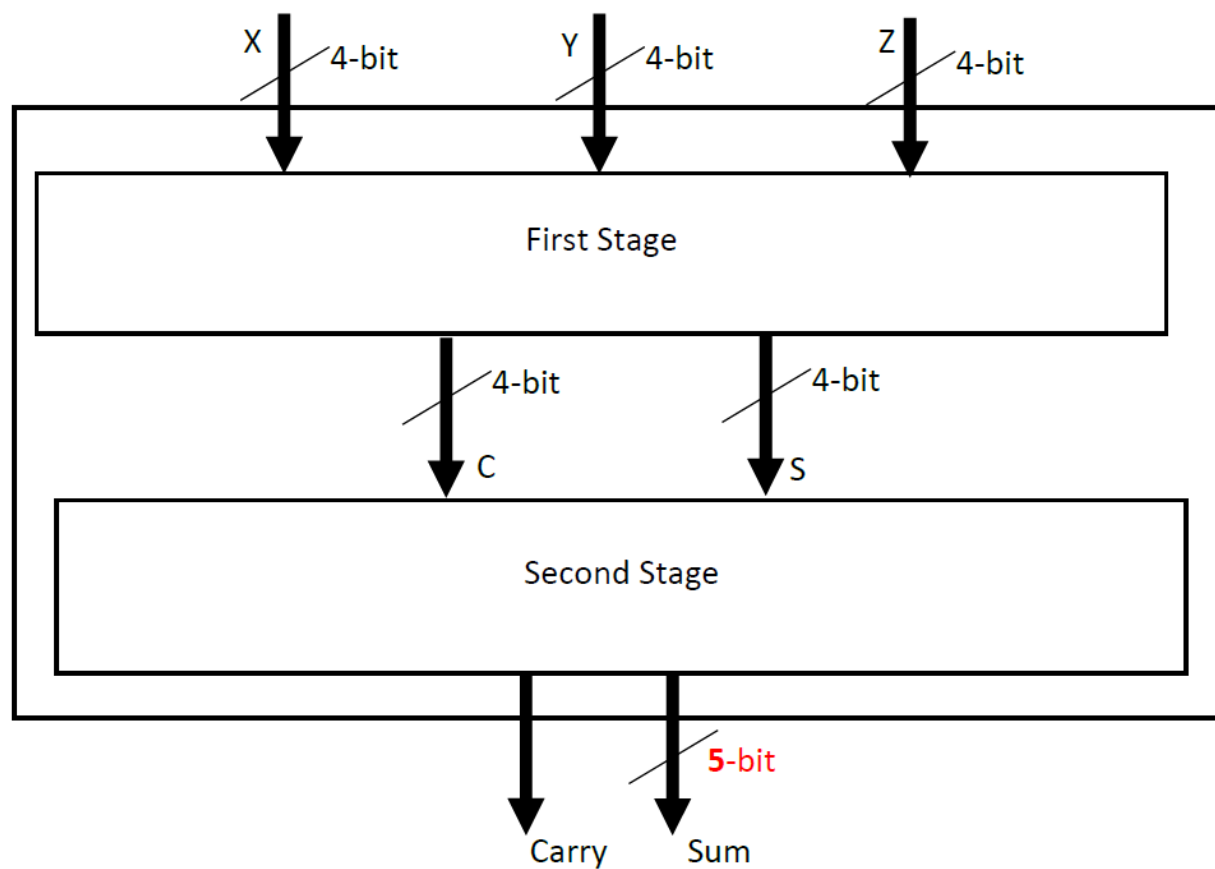- 1- In the first stage, we need to reduce the problem of adding three numbers into adding two  $n$ -bit numbers. The 8-bits of S and C will be computed at the same time.
- 2- In the second stage, RCA is used to compute the summation and the carry.



- In the first stage, I will determine C and S vectors, so that each bit in the S vector represents the sum of one bit of each input vectors in the same order, and each bit in the C vector represents the carry of that sum.

This example shows the process:


If we consider that  $X = "1010"$ ,  $Y = "1110"$  and  $Z = "0001"$

We find that  $S = "0101"$  and  $C = "1010"$ .

<b>X</b>	1	0	1	0
<b>Y</b>	1	1	1	0
<b>Z</b>	0	0	0	1
<b>S</b>	0	1	0	1
<b>C</b>	1	0	1	0

For first bit at the right  $0+0+1$  this will equal 01 ( $s=1, c=0$ )

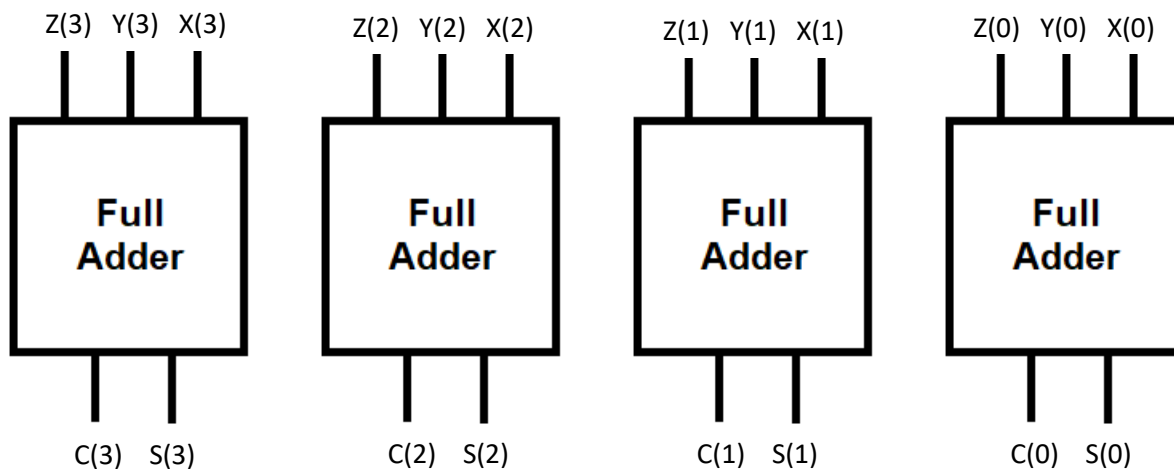This stage can be done by Full Adder for each bit.



- In the second stage I will sum S vector with C vector but before do this I will add a bit with value zero at the right of C vector to achieve a correct result for sum, to clarify the process, we did the following:

We determined the S and C vectors from the first stage, suppose we get this result:


S= "0110" and C= "1011" then

The calculation will be this

$$\begin{array}{r}
 0110 + \\
 1011 \text{ } 0 \\
 \hline
 011100
 \end{array}$$

carry      Sum

This stage can be done by RCA.

 

- To implement this application on VHDL we will first create entity for Half and full Adder

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity HA is
5  port(a,b : in std_logic;
6       sum,cout : out std_logic);
7  end entity;
8
9  architecture HA_arch of HA is
10 begin
11     sum<= a xor b;
12     cout<= a and b;
13 end architecture;
14

```

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity FA is
5  port(a, b, cin : in std_logic;
6       sum, cout: out std_logic);
7  end entity;
8
9  architecture FA_arch of FA is
10
11     component HA is
12     port(a,b: in std_logic;
13          sum,cout: out std_logic);
14     end component;
15
16     signal sum1, cout1, cout2 :std_logic;
17
18     begin
19
20         HF1 : HA port map(a,b,sum1,cout1);
21         HF2 : HA port map(sum1,cin,sum,cout2);
22
23         cout<= cout1 or cout2;
24
25     end architecture;

```

And then we create our application:

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity stage1 is
5  port(x, y, z : in std_logic_vector(3 downto 0);
6       s, c : out std_logic_vector(3 downto 0));
7  end entity;
8
9  architecture stage1_arch of stage1 is
10
11  component FA is
12  port(a, b, cin : in std_logic;
13       sum, cout: out std_logic);
14  end component;
15
16  begin
17
18  FA1 : FA port map(x(0),y(0),z(0),s(0),c(0));
19  FA2 : FA port map(x(1),y(1),z(1),s(1),c(1));
20  FA3 : FA port map(x(2),y(2),z(2),s(2),c(2));
21  FA4 : FA port map(x(3),y(3),z(3),s(3),c(3));
22
23  end architecture;
```

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity stage2 is
5  port(s, c: in std_logic_vector(3 downto 0);
6       sum: out std_logic_vector(4 downto 0);
7       carry: out std_logic);
8  end entity;
9
10 architecture stage2_arch of stage2 is
11
12  component FA is
13  port(a, b, cin : in std_logic;
14       sum, cout: out std_logic);
15  end component;
16
17  signal cout1, cout2, cout3: std_logic;
18
19  begin
20
21  sum(0) <= s(0);
22  FA1 : FA port map(s(1),c(0) , '0' ,sum(1),cout1);
23  FA2 : FA port map(s(2),c(1) ,cout1,sum(2),cout2);
24  FA3 : FA port map(s(3),c(2) ,cout2,sum(3),cout3);
25  FA4 : FA port map(c(3),cout3,'0' ,sum(4),carry);
26
27
28  end architecture;
```

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity Three_Number_Adder is
5  port(x, y, z : in std_logic_vector(3 downto 0);
6       sum : out std_logic_vector(4 downto 0);
7       carry : out std_logic);
8  end entity;
9
10 architecture Three_Number_Adder_arch of Three_Number_Adder is
11
12  component stage1 is
13  port(x, y, z : in std_logic_vector(3 downto 0);
14       s, c : out std_logic_vector(3 downto 0));
15  end component;
16
17  component stage2 is
18  port(s, c : in std_logic_vector(3 downto 0);
19       sum: out std_logic_vector(4 downto 0);
20       carry: out std_logic);
21  end component;
22
23  signal s, c: std_logic_vector(3 downto 0);
24
25
26  begin
27
28  stage1_o: stage1 port map (x, y, z, s, c);
29  stage2_o: stage2 port map (s, c, sum, carry);
30
31  end architecture;
```

**Test Bench:** For simplicity, the Test bench can be conducted using three different tuples only (e.g., T1= (X= 1100, Y= 1101, Z=1110), T2= (X= 1111, Y= 1000, Z= 1001), T3= (X= 1110, Y= 0101, Z= 0111)).

- To test my solution:

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity Three_Number_Adder_TB is
5  end entity;
6
7  architecture Three_Number_Adder_TB_arch of Three_Number_Adder_TB is
8
9  component Three_Number_Adder is
10 port(x, y, z : in std_logic_vector(3 downto 0);
11      sum : out std_logic_vector(4 downto 0);
12      carry : out std_logic);
13 end component;
14
15 signal x_TB, y_TB, z_TB: std_logic_vector(3 downto 0);
16 signal sum_TB: std_logic_vector(4 downto 0);
17 signal carry_TB: std_logic;
18
19 begin
20
21 Three_Number_Adder_1: Three_Number_Adder port map(x_TB, y_TB, z_TB, sum_TB, carry_TB);
22
23 STIMULUS : process
24 begin
25
26 x_TB <= "1100" ; y_TB <= "1101" ; z_TB <= "1110" ; wait for 20 ns;
27 x_TB <= "1111" ; y_TB <= "1000" ; z_TB <= "1001" ; wait for 20 ns;
28 x_TB <= "1110" ; y_TB <= "0101" ; z_TB <= "0111" ; wait for 20 ns;
29
30 end process;
31 end architecture;

```

Signal	Value 1	Value 2	Value 3
/three_number_add... x_TB	1100	1111	1110
/three_number_add... y_TB	1101	1000	0101
/three_number_add... z_TB	1110	1001	0111
/three_number_add... sum_TB	00111	00000	11010
/three_number_add... carry_TB	1		

done